

Richiami di teoria dei circuiti - Esercizi

Problem: Thevenin Models

Draw Thevenin Models for the following circuits. Give answers to 10% and to 1%

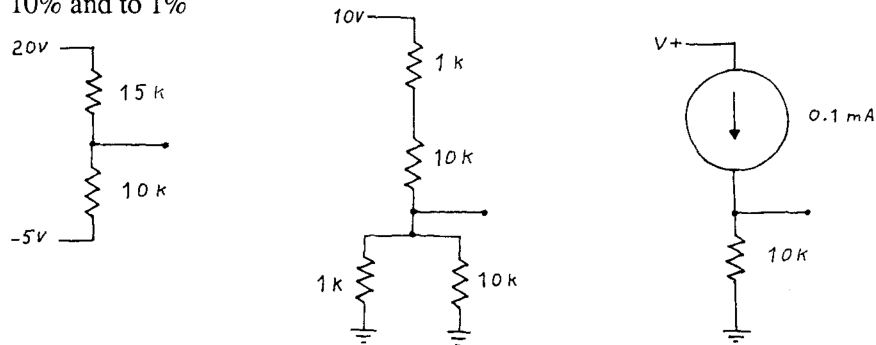


Figure X1.6: Some circuits to be reduced to Thevenin models

Problem: R_{in} , R_{out}

What are R_{in} , R_{out} at the indicated points?

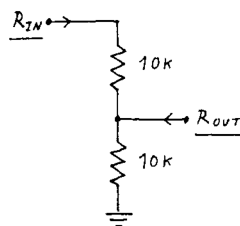


Figure X1.10: Determining R_{in} , R_{out} ; you need to decide what's beyond the circuit to which you're connecting